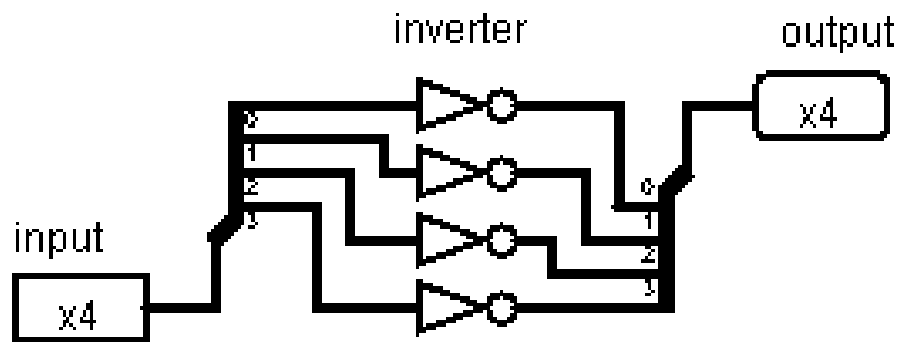


## Lab1 - Bitwise Not Circuit

Jun ho Lim



### Description

A 4-bit Bitwise Not Circuit.